

# Digital Design Lab Report

<b>Name</b>	Dev Goel
<b>Roll No.</b>	B20CS090
<b>Experiment Number</b>	V

## Objective

- (i) Write a program to implement a Barrel Shifter.
- (ii) Write a Program to implement a 32-bit ALU.
- (iii) Write a program to implement a 4-line to 2-line priority encoder using
  - a. Casex statements
  - b. For loop
- (iv) Write a behavioural code for implementing
  - a. A BCD Adder/Subtractor Unit.
  - b. Multiply by 5 circuit.

**EXPERIMENT (i):** Write a program to implement a Barrel Shifter.

### Barrel Shifter:

```
`timescale 1ns / 1ps
module barrel_shifter(inp_w, inp_s, out_y);

input [3:0] inp_w;
input [1:0] inp_s;
output [3:0] out_y;

mux41 m1(inp_w[3], inp_w[0], inp_w[1], inp_w[2], inp_s[0], inp_s[1],
out_y[3]);
mux41 m2(inp_w[2], inp_w[3], inp_w[0], inp_w[1], inp_s[0], inp_s[1],
out_y[2]);
```

```

mux41 m3(inp_w[1], inp_w[2], inp_w[3], inp_w[0], inp_s[0], inp_s[1],
out_y[1]);
mux41 m4(inp_w[0], inp_w[1], inp_w[2], inp_w[3], inp_s[0], inp_s[1],
out_y[0]);

endmodule

```

#### **4\*1 Multiplexer:**

```

`timescale 1ns / 1ps
module mux41(input a, input b, input c, input d, input s0, s1, output out);

assign out = s1 ? (s0 ? d : c) : (s0 ? b : a);

endmodule

```

#### **Test Bench:**

```

`timescale 1ns / 1ps
module test_barrel_shifter;

reg [3:0] inp_w;
reg [1:0] inp_s;
wire [3:0] out_y;
integer i;

barrel_shifter bs1(inp_w, inp_s, out_y);



initial
begin
    for(i = 1; i < 16; i=i+1)
    begin
        assign inp_w = i;
        inp_s[1] = 0;
        inp_s[0] = 0; #10;
        inp_s[1] = 0;
        inp_s[0] = 1; #10;
    end
end

```

```
inp_s[1] = 1;
inp_s[0] = 0; #10;
inp_s[1] = 1;
inp_s[0] = 1; #10;
end
end
initial #600 $finish;

endmodule
```

Waveform:

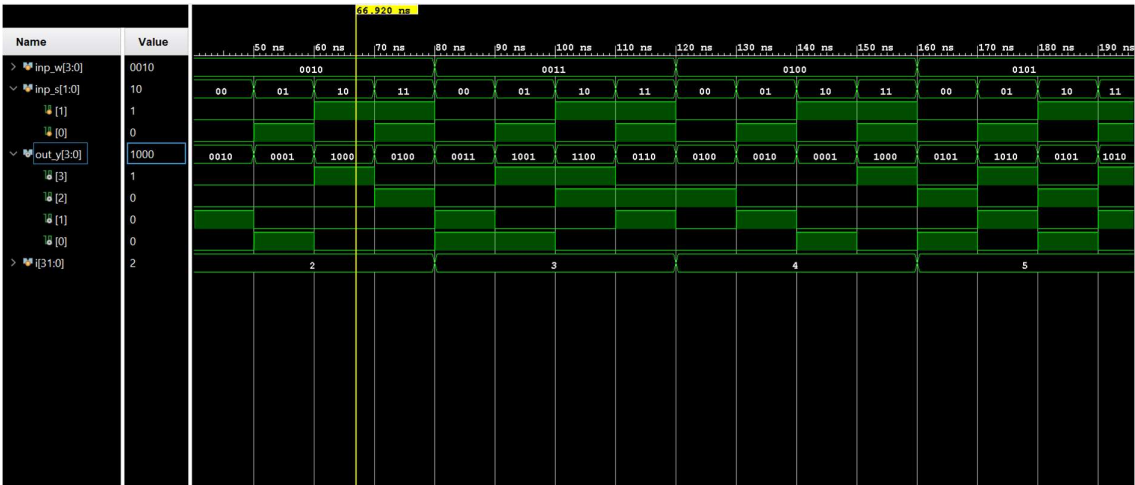 

**EXPERIMENT (ii):** Write a Program to implement a 32-bit ALU.

**32-bit ALU:**

```
`timescale 1ns / 1ps
module alu(inp_a, inp_b, operator, out_ans);
```

```
input [31:0] inp_a, inp_b;
```

```
input [2:0] operator;
```

```
output reg [31:0] out_ans;
```

```
always @*
```

```
begin
```

```
    case(operator)
```

```
        // Clear
```

```
        0: out_ans = 0;
```

```
        // Addition
```

```
        1: out_ans = inp_a + inp_b;
```

```
        // Subtraction
```

```
        2: out_ans = inp_a - inp_b;
```

```
        // Left shift
```

```
        3: out_ans = inp_a << 1;
```

```
        // Right Shift
```

```
        4: out_ans = inp_a >> 1;
```

```
        // A AND B
```

```
        5: out_ans = inp_a & inp_b;
```

```

        // A OR B

        6: out_ans = inp_a | inp_b;

        // A XOR B

        7: out_ans = inp_a ^ inp_b;

    endcase

end

endmodule

```

### **Test Bench:**

```

`timescale 1ns / 1ps
module test_alu;


    reg [31:0] inp_a, inp_b;
    reg [2:0] operator;
    wire [31:0] out_ans;

    alu alu1(inp_a, inp_b, operator, out_ans);
    initial
        begin
            inp_a = 24;
            inp_b = 8;
            operator = 0; #10;
            operator = 1; #10;
            operator = 2; #10;
            operator = 3; #10;
            operator = 4; #10;
            operator = 5; #10;
            operator = 6; #10;
            operator = 7; #10;
        end

    initial #80 $finish;
endmodule

```

## Waveform:

 

**EXPERIMENT (iii) a:** Write a program to implement a 4-line to 2-line priority encoder using casex statements

### - Priority Encoder (Using Casex Statements):

```
`timescale 1ns / 1ps
module priority_encoder_casex(inp_D, out_X);
```

```
input [3:0] inp_D;
output reg [1:0] out_X;
reg V;
```

```
always@(inp_D)
begin
    V = 1;
    case(inp_D)
        4'b1XXX: out_X = 2'b11;
        4'b01XX: out_X = 2'b10;
```

```

    4'b001X: out_X = 2'b01;
    4'b0001: out_X = 2'b00;
    default:
        begin V = 0;
            out_X = 2'bXX;
        end
    endcase
end
endmodule

```

### **Test Bench:**

```

`timescale 1ns / 1ps
module test_priority_encoder_casex;

    reg [3:0] inp_D;
    wire [1:0] out_X;

    priority_encoder_casex pec(inp_D, out_X);

    initial
        begin
            inp_D = 4'b0000; #10;
            inp_D = 4'b0001; #10;
            inp_D = 4'b001X; #10;
            inp_D = 4'b01XX; #10;
            inp_D = 4'b1XXX; #10;
        end

    initial #50 $finish;
endmodule

```

## Waveform:



**EXPERIMENT (iii) b:** Write a program to implement a 4-line to 2-line priority encoder using for loop.

- **Priority Encoder (Using for loop):**

```
`timescale 1ns / 1ps
module priority_encoder_for_loop(inp_D, out_X);
```

```
output reg [1:0] out_X;
input [3:0] inp_D;
reg V;
integer i;
```

```
always@(inp_D)
begin
    out_X = 2'bXX;
    V = 0;
```



```

        for(i = 0; i < 4; i = i + 1)
            begin
                if(inp_D[i])
                    begin
                        out_X = i;
                        V = 1;
                    end
            end
        end
    end
endmodule

```

### **Test Bench:**

```

`timescale 1ns / 1ps
module test_priority_encoder_for_loop;

    reg [3:0] inp_D;
    wire [1:0] out_X;

    priority_encoder_for_loop pefl(inp_D, out_X);

    initial
        begin
            inp_D = 4'b0000; #10;
            inp_D = 4'b0001; #10;
            inp_D = 4'b001X; #10;
            inp_D = 4'b01XX; #10;
            inp_D = 4'b1XXX; #10;
        end

    initial #50 $finish;
endmodule

```

## Waveform:



**EXPERIMENT (iv) a:** Write a behavioural code for implementing a BCD Adder/Subtractor Unit.

### - BCD Adder:

```
`timescale 1ns / 1ps
module bcd_adder(inp_a, inp_b, carry_in, sum, carry);

input [3:0] inp_a, inp_b;
input carry_in;
output [3:0] sum;
output carry;
reg [4:0] sum_temp;
reg [3:0] sum;
reg carry;

always @(inp_a, inp_b, carry_in)
begin
    sum_temp = inp_a + inp_b + carry_in;
    if(sum_temp > 9)
```

```

        begin
            sum_temp = sum_temp+6;
            carry = 1;
            sum = sum_temp[3:0];
        end
    else
        begin
            carry = 0;
            sum = sum_temp[3:0];
        end
    end
end

endmodule

```

### **Test Bench:**

```

`timescale 1ns / 1ps
module test_bcd_adder;

reg [3:0] inp_a;
reg [3:0] inp_b;
reg carry_in;
wire [3:0] sum;
wire carry;

bcd_adder bcda(inp_a, inp_b, carry_in, sum, carry);

initial
begin
    inp_a = 0; inp_b = 0; carry_in = 0; #10;
    inp_a = 6; inp_b = 9; #10;
    inp_a = 3; inp_b = 3; #10;
    inp_a = 4; inp_b = 5; #10;
    inp_a = 8; inp_b = 2; #10;
    inp_a = 9; inp_b = 9; carry_in = 1; #10;
    inp_a = 0; inp_b = 0; #10;
    inp_a = 6; inp_b = 9; #10;

```

```

inp_a = 3; inp_b = 3; #10;
inp_a = 4; inp_b = 5; #10;
inp_a = 8; inp_b = 2; #10;
inp_a = 9; inp_b = 9; #10;
end


```

```

initial #120 $finish;
endmodule

```

### Waveform:

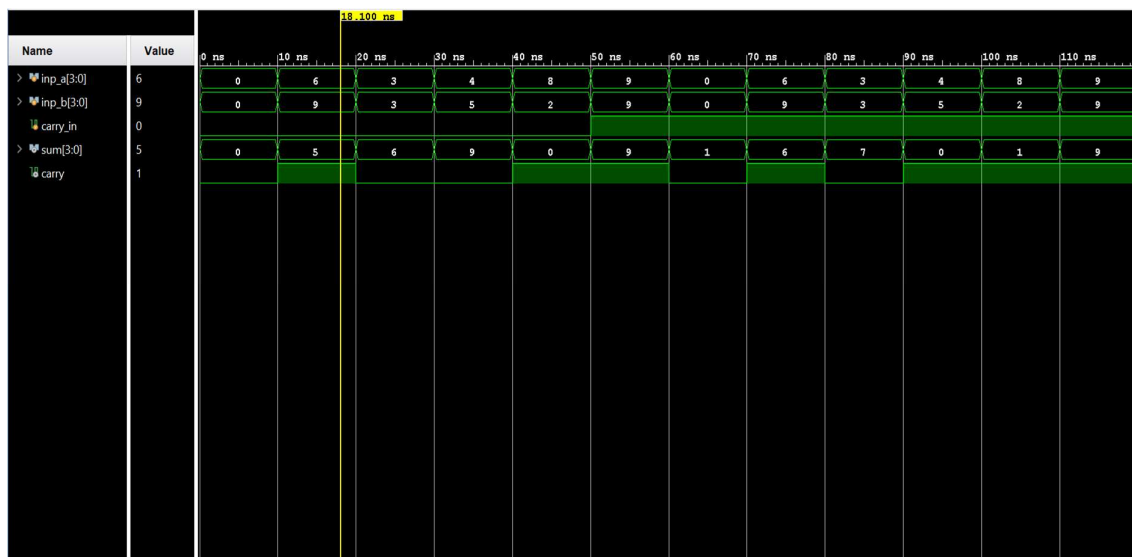

### - BCD Subtractor:

```

`timescale 1ns / 1ps
module bcd_subtractor(inp_a, inp_b, diff, carry);

input [3:0] inp_a, inp_b;
output [3:0] diff;
output carry;
reg [4:0] diff_temp;
reg [3:0] diff;
reg carry;

```

```

always @(inp_a, inp_b)
begin
    diff_temp = inp_a + 10 - inp_b;
    if(diff_temp > 9)
        begin
            diff_temp = diff_temp+6;
            carry = 1;
            diff = diff_temp[3:0];
        end
    else
        begin
            carry = 0;
            diff = diff_temp[3:0];
            diff = 10-diff;
        end
    end
end
endmodule

```

### **Test Bench:**

```

`timescale 1ns / 1ps
module test_bcd_subtractor;

    reg [3:0] inp_a;
    reg [3:0] inp_b;
    wire [3:0] diff;
    wire carry;


    bcd_subtractor bcds(inp_a, inp_b, diff, carry);

    initial
    begin
        inp_a = 0; inp_b = 0; #10;
    end
endmodule

```

```
inp_a = 6; inp_b = 9; #10;
inp_a = 3; inp_b = 3; #10;
inp_a = 4; inp_b = 5; #10;
inp_a = 8; inp_b = 2; #10;
inp_a = 9; inp_b = 9; #10;
inp_a = 0; inp_b = 0; #10;
inp_a = 6; inp_b = 9; #10;
inp_a = 3; inp_b = 3; #10;
inp_a = 4; inp_b = 5; #10;
inp_a = 8; inp_b = 2; #10;
inp_a = 9; inp_b = 9; #10;
end
initial #120 $finish;
endmodule
```

**Waveform:**

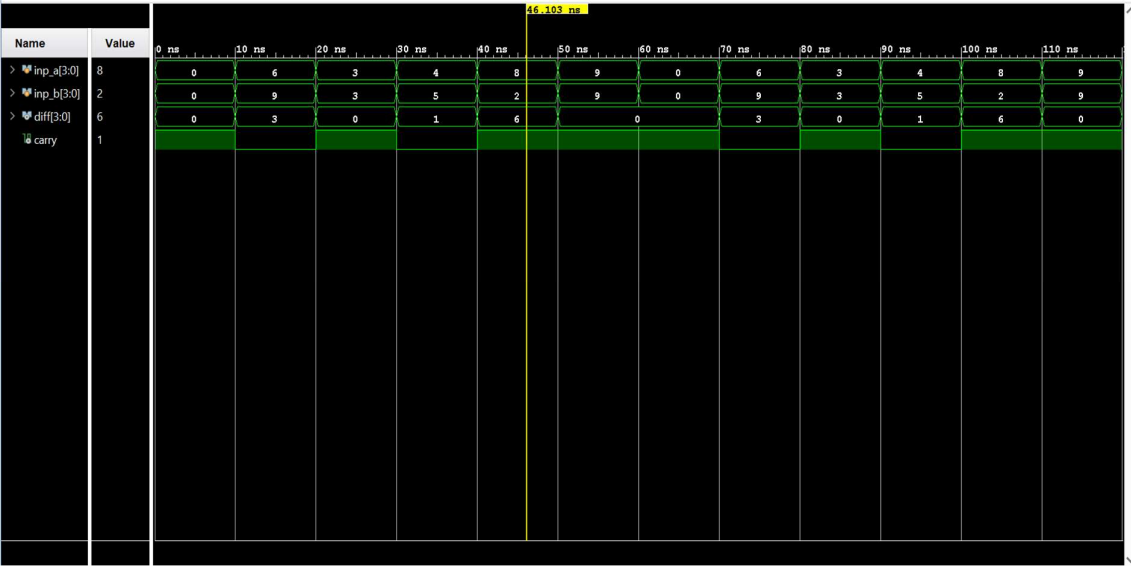

**EXPERIMENT (iv) b:** Write a behavioural code for implementing a Multiply by 5 circuit.

**Multiply by 5 circuit:**

```
`timescale 1ns / 1ps
module multiplication_by_5(inp_a, out_b);

input [3:0] inp_a;
output reg[6:0] out_b;
reg [5:0] sum1;
reg [3:0] sum2;

always@*
begin
    assign sum2 = inp_a;
    assign sum1 = inp_a << 2;
    assign out_b = sum1 + sum2;
end
endmodule
```

**Test Bench:**

```
`timescale 1ns / 1ps
module test_multiplication_by_5;

reg [3:0] inp_a;
wire [6:0] out_b;
integer i;
```

```
multiplication_by_5 mb5(inp_a, out_b);
```

```
initial
begin
    for(i = 0; i < 16; i=i+1)
        begin
            assign inp_a = i; #10;
        end
    end
end
```

```
initial #160 $finish;
endmodule
```

**Waveform:**

