

# Digital Design Lab Report

<b>Name</b>	Dev Goel
<b>Roll No.</b>	B20CS090
<b>Experiment Number</b>	<b>II</b>

## Objective

- (i) Write a program to implement (with test benches).
  - a.) Binary to Gray Code Converter.
  - b.) Gray code to Binary code Converter.
- (ii) Write a program to implement a BCD to 7-segment display decoder.
- (iii) Implement a Buzzer system in Verilog. Write test bench and verify various cases.

**Work 1a:** Write a program to implement Binary to Gray Code converter. Write its test bench and simulate.

### - Binary to Gray Code

```
`timescale 1ns / 1ps
```

```
module binary_to_gray(input [0:3] bin, output [0:3] Gray);
```

```
    assign Gray[0] = bin[0];
```

```
    assign Gray[1] = bin[0] ^ bin[1];
```

```
    assign Gray[2] = bin[1] ^ bin[2];
```

```
    assign Gray[3] = bin[2] ^ bin[3];
```

```
endmodule
```

## - Test Bench

```
`timescale 1ns / 1ps


module test_binary_to_gray;

reg [0:3] bin;
wire [0:3] Gray;

binary_to_gray b2g(bin, Gray);

always
begin
    bin = 0;
    #10 bin = 1;
    #10 bin = 2;
    #10 bin = 3;
    #10 bin = 4;
    #10 bin = 5;
    #10 bin = 6;
    #10 bin = 7;
    #10 bin = 8;
    #10 bin = 9;
    #10 bin = 10;
    #10 bin = 11;
    #10 bin = 12;
    #10 bin = 13;
    #10 bin = 14;
    #10 bin = 15;
    #10;
    $stop;
end
endmodule
```

## - Waveform

 

**Work 1b:** Write a program to implement Gray Code to Binary converter. Write its test bench and simulate.

- **Gray Code to Binary**

```
`timescale 1ns / 1ps

module gray_to_binary(input [0:3] G, output [0:3] bin);

    assign bin[0] = G[0];
    assign bin[1] = G[0] ^ G[1];
    assign bin[2] = G[0] ^ G[1] ^ G[2];
    assign bin[3] = G[0] ^ G[1] ^ G[2] ^ G[3];

endmodule
```

- **Test Bench**

```
`timescale 1ns / 1ps

module test_gray_to_binary;

    reg [0:3] Gray;
    wire [0:3] bin_out;

    gray_to_binary g2b(Gray, bin_out);


    always
    begin
        Gray = 0;
        #10 Gray = 1;
    end
endmodule
```

```

#10 Gray = 3;
#10 Gray = 2;
#10 Gray = 6;
#10 Gray = 7;
#10 Gray = 5;
#10 Gray = 4;
#10 Gray = 12;
#10 Gray = 13;
#10 Gray = 15;
#10 Gray = 14;
#10 Gray = 10;
#10 Gray = 11;
#10 Gray = 9;
#10 Gray = 8;
#10;
$stop;
end
endmodule

```

## - Waveform

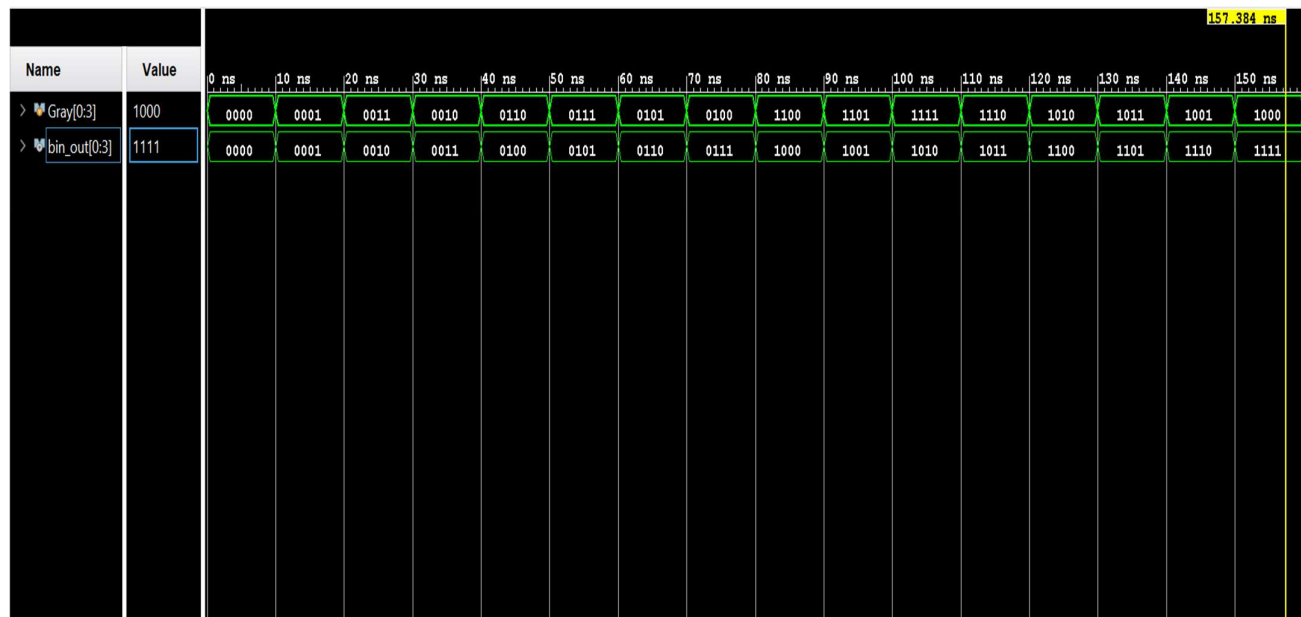

**Work 2:** Write a program to implement a BCD to 7-segment display decoder.

- **Four Bit Adder**

```
`timescale 1ns / 1ps
module bcd_to_seven(bcd, sevenSeg);

input [0:3] bcd;
output [0:6] sevenSeg;
reg [0:6] sevenSeg;

always @(bcd)
begin
    case (bcd)
        0 : sevenSeg = 7'b1111110;
        1 : sevenSeg = 7'b0110000;
        2 : sevenSeg = 7'b1101101;
        3 : sevenSeg = 7'b1111001;
        4 : sevenSeg = 7'b0110011;
        5 : sevenSeg = 7'b1011011;
        6 : sevenSeg = 7'b1011111;
        7 : sevenSeg = 7'b1110000;
        8 : sevenSeg = 7'b1111111;
        9 : sevenSeg = 7'b1111011;
        default : sevenSeg = 7'b0000000;
    endcase
end

endmodule
```

**Work 3:** Implement a Buzzer system in Verilog. Write test bench and verify various cases.

- **Buzzer**

```
`timescale 1ns / 1ps
module buzzer(inp_a, inp_b, control, out_a, out_b);

input inp_a, inp_b, control;
output out_a, out_b;
wire p, q;

assign p = inp_a && control;
assign q = inp_b && control;

bufif0(out_a, p, q);
bufif0(out_b, q, p);

endmodule
```

- **Test Bench**

```
module test_buzzer();

reg inp_a, inp_b, control;
wire out_a, out_b;

buzzer bz(inp_a, inp_b, control, out_a, out_b);
initial
    begin
```

```

inp_a = 0; inp_b = 0; control = 0;
#10 inp_a = 1; inp_b = 0; control = 0;
#10 inp_a = 1; inp_b = 0; control = 1;
#10 inp_a = 1; inp_b = 0; control = 0;
#10 inp_a = 0; inp_b = 1; control = 1;
end
initial #60 $finish;
endmodule

```

## - Waveform

