

# Digital Design Lab Report

<b>Name</b>	Dev Goel
<b>Roll No.</b>	B20CS090
<b>Experiment Number</b>	<b>VIII</b>

## Objective

- (i) Create the 8bit MLS counter using LFSR.
- (ii) Write a program to implement 2's complement of a running bit stream using
  - a. Melay Machine
  - b. Moore Machine

Use LFSR for generating input bit stream.

**EXPERIMENT (i):** Create the 8bit MLS counter using LFSR.

```
`timescale 1ns / 1ps
module MLS_Counter(clk, lfsr);

input clk;
output reg [7:0] lfsr = 42;

wire w1 = lfsr[3];
wire w2 = lfsr[2];
wire w3 = lfsr[1];
wire w4 = lfsr[7];

always@(posedge clk)
begin
    lfsr[7:1] <= lfsr[6:0];
    lfsr[0] <= lfsr[3]^lfsr[4]^lfsr[5]^lfsr[7];
end
```

```

    end
endmodule

```

### Test Bench:

```

`timescale 1ns / 1ps
module MLS_Counter_test;

reg clk;
wire [7:0] lfsr;

MLS_Counter mls(clk, lfsr);


initial begin
    clk = 0;
end

always #10 clk = ~clk;

initial #180 $finish;
endmodule

```

### Waveform:

 

**EXPERIMENT (ii) a:** Write a program to implement 2's complement of a running bit stream using Melay Machine.

```
`timescale 1ns / 1ps
module melay_machine_2_complement(clk, rst, a, out, ps, ns);

input clk, rst;
input a;

output reg out;
output reg ps, ns;

parameter s0 = 1'b0;
parameter s1 = 1'b1;

always@(posedge clk, negedge rst)
begin
    if(!rst)
        ps <= s0;
    else
        ps <= ns;
end

always@(ps, a)
begin
    case(ps)
    s0: if(a)
        begin
            ns <= s1;
            out <= 1;
        end
    else
        begin
            ns <= s0;
            out <= 0;
        end
    s1: if(a)
```

```

        begin
            out <= 0;
            ns <= s1;
        end
    else
        begin
            out <= 1;
            ns <= s1;
        end
    endcase
end
endmodule

```

### **Test Bench:**

```

`timescale 1ns / 1ps
module test_melay_machine_2_complement;

reg clk, reset;
reg a;
wire out;
wire ps, ns;

melay_machine_2_complement mem2c(clk, reset, a, out, ps, ns);

always #5 clk = ~clk;


initial
    begin
        clk = 0;
        reset = 0;
        a = 1;
        #10 reset = 1;
        #10 a = 0;
        #10 a = 1;
        #10 a = 1;
    end

```

```
#10 a = 0;
#10 a = 1;
#10 a = 0;
#10 a = 1;
#10 a = 1;
#10 a = 1;
end

initial #110 $finish;
endmodule
```

## Waveform:

 

**EXPERIMENT (ii) b:** Write a program to implement 2's complement of a running bit stream using Moore Machine.

```
`timescale 1ns / 1ps
module moore_machine_2_component(clk, reset, a, out, state);

input clk, reset, a;
output reg out;
output reg [1:0] state;

integer i;
parameter s0 = 2'b00, s1 = 2'b01, s2 = 2'b10;

always @(posedge clk, negedge reset)
begin
    if(!reset)
        state<=s0;
    else
        begin
            case(state)
            s0:if(!a)
                state<=s0;
            else
                state<=s1;
            s1:if(!a)
                state<=s1;
            else
                state<=s2;
            s2:if(!a)
                state<=s1;
            else
                state<=s2;
            endcase
        end
end

always @(state)
```

```
begin
    case(state)
    s0: out<=0;
    s1: out<=1;
    s2: out<=0;
    endcase
end
```

```
endmodule
```

### **Test Bench:**

```
`timescale 1ns / 1ps
module test_moore_machine_2_complement();

reg clk ,reset;
reg a;
wire out;
wire [1:0] state;
moore_machine_2_component mom2c(clk, reset, a, out, state);

always #5 clk = ~clk;

initial begin
    clk = 0;
    reset = 0;
    a = 1;
    #10 reset = 1;
    #10 a = 0;
    #10 a = 1;
    #10 a = 1;
    #10 a = 0;
    #10 a = 1;
    #10 a = 0;
end
initial #80 $finish;
endmodule
```

Waveform:

